

# FIT1047 – Week 3

## Central Processing Units

(part 2)

# Recap

In the previous lecture we saw

- Basic CPU architecture
- MARIE assembly code
- Combinational circuits (adders, MUXes, decoders)
- ALUs

# Overview

- Sequential Circuits
  - flip flops, registers, counters
  - memory
- Control
  - executing a program

# Sequential Circuits

# Sequential Circuits

(output depends on sequence  
of inputs)

# Sequences

How can a circuit remember the past?

# Sequences

How can a circuit remember the past?

Feed the output back into the input!

# Sequences

How can a circuit remember the past?

Feed the output back into the input!



# Sequences

How can a circuit remember the past?

Feed the output back into the input!

Let's add a switch to control the state.

# Sequences

How can a circuit remember the past?

Feed the output back into the input!

# Sequences

How can a circuit remember the past?

Feed the output back into the input!

# Sequences

How can a circuit remember the past?

Feed the output back into the input!

Can we implement a toggle?

# Sequences

# Sequences

# Sequences

This is called an SR latch (set-reset-latch).

# SR Latch

Truth table:

S	R	$Q(t)$	$Q(t+1)$
0	0	0	0
0	1	0	1
1	0	0	0
1	1	forbidden	
0	0	1	1
0	1	1	1
1	0	1	0
1	1	forbidden	



# SR Latch

Truth table:

S	R	$Q(t)$	$Q(t+1)$
0	0	0	0
0	1	0	1
1	0	0	0
1	1	forbidden	
0	0	1	1
0	1	1	1
1	0	1	0
1	1	forbidden	


But digital circuits use a single input (bit).

# D flip-flop

- One input: the data to be stored
- One output: the data currently stored
- Plus a clock: state only changes on "positive edge"
 
# D flip-flop

- One input: the data to be stored
- One output: the data currently stored
- Plus a clock: state only changes on "positive edge"



# Registers

# Registers

- Very fast memory inside the CPU

# Registers

- Very fast memory inside the CPU
- Some special purpose registers
  - PC, IR, MBR, MAR (for MARIE)

# Registers

- Very fast memory inside the CPU
- Some special purpose registers
  - PC, IR, MBR, MAR (for MARIE)
- Some general purpose registers
  - AC (MARIE), AH/AL, BH/BL, CH/CL, DH/DL (x86)

# Registers

- Very fast memory inside the CPU
- Some special purpose registers
  - PC, IR, MBR, MAR (for MARIE)
- Some general purpose registers
  - AC (MARIE), AH/AL, BH/BL, CH/CL, DH/DL (x86)
- Fixed bit width
  - e.g. 16 bits in MARIE, 16/32 or 64 bits in modern processors



# Register file

# Register file

- Collection of registers

# Register file

- Collection of registers
- Each implemented using  $n$  flip-flops (for  $n$  bits)

# Register file

- Collection of registers
- Each implemented using  $n$  flip-flops (for  $n$  bits)
- $n$  inputs and outputs

# Register file


- Collection of registers
- Each implemented using  $n$  flip-flops (for  $n$  bits)
- $n$  inputs and outputs
- Additional input: select register for writing

# Register file

- Collection of registers
- Each implemented using  $n$  flip-flops (for  $n$  bits)
- $n$  inputs and outputs
- Additional input: select register for writing
- Additional input: select register for reading


# Register file

# Register file

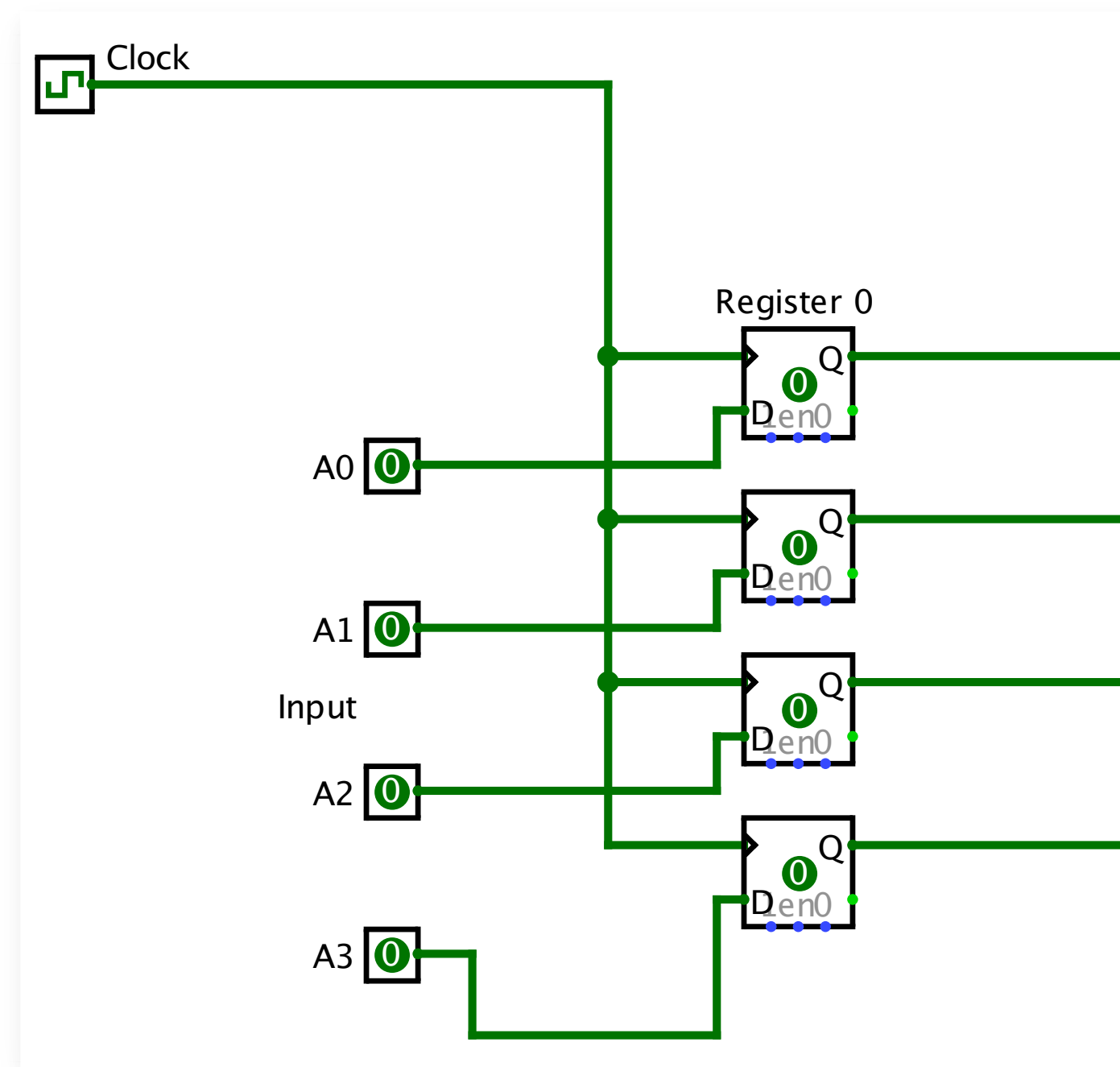





# Register file

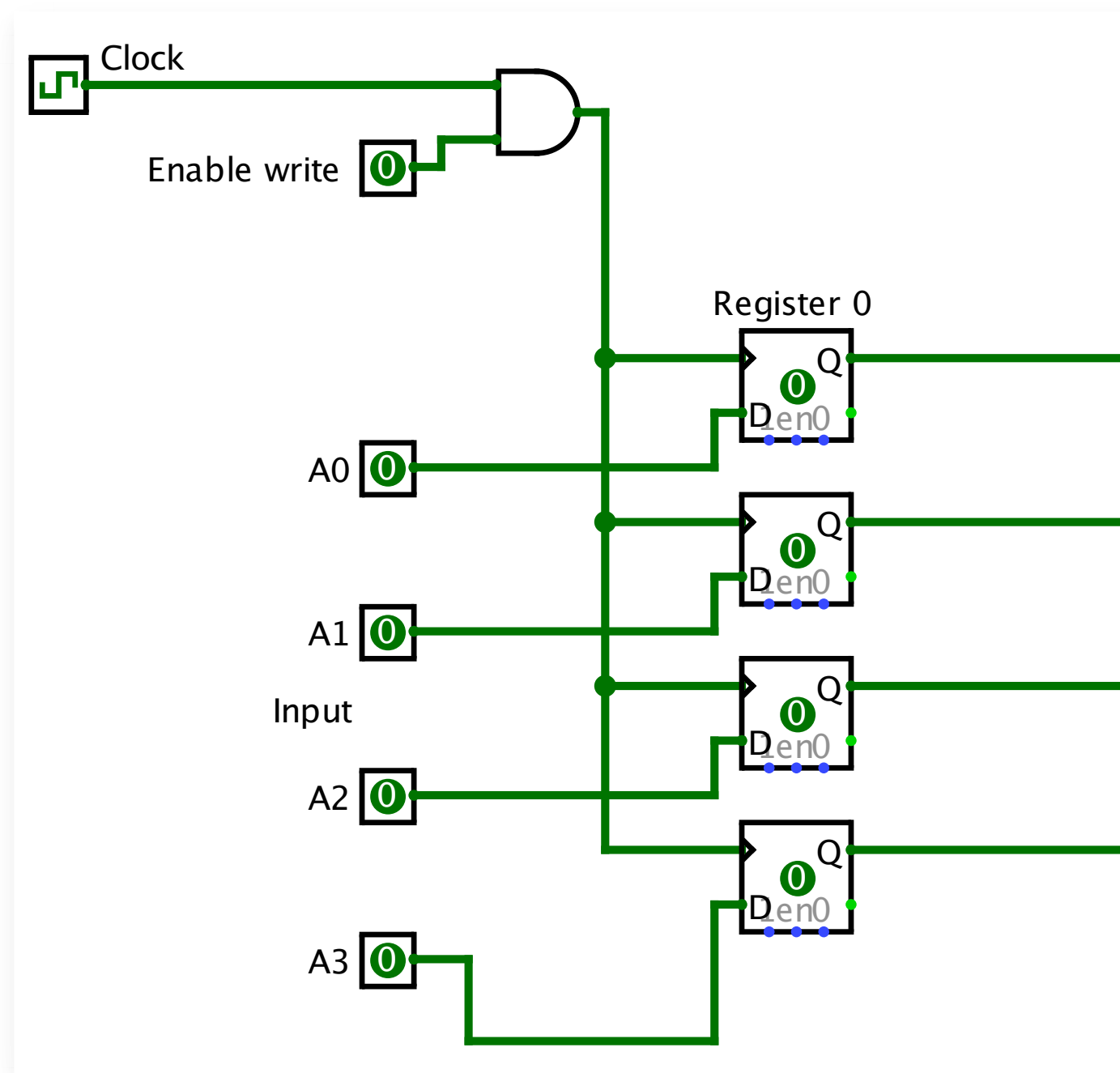


# Register file

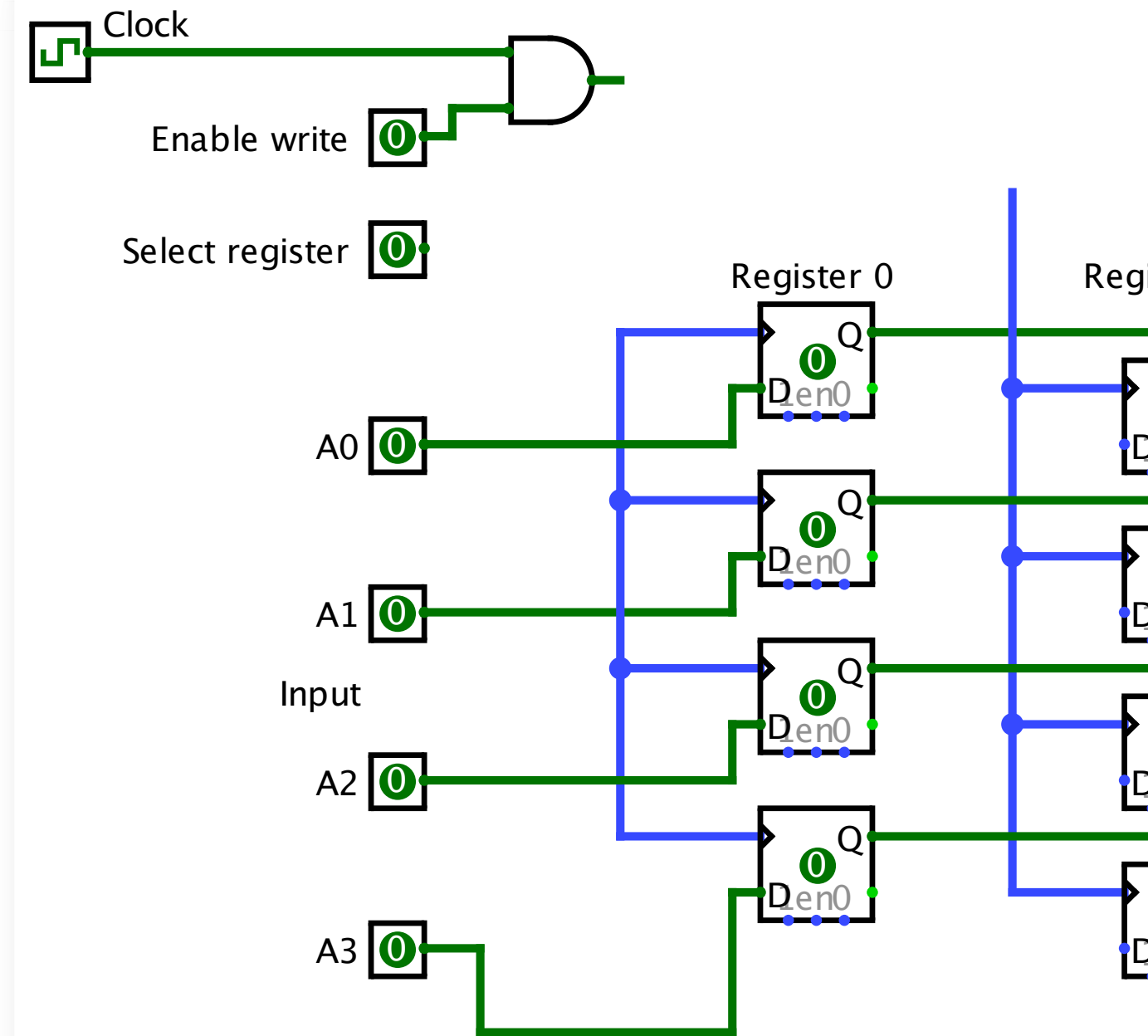


# Register file

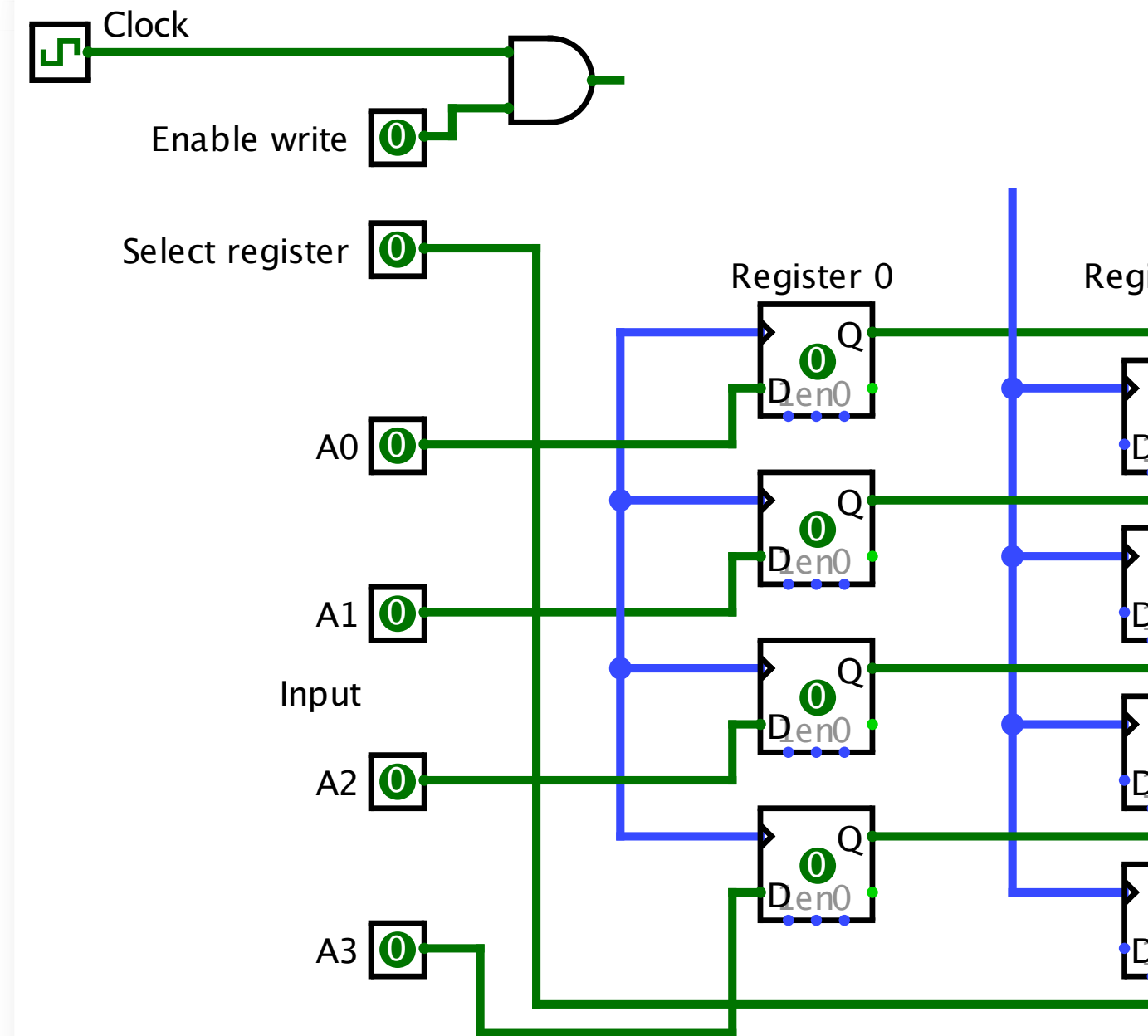

# Register file

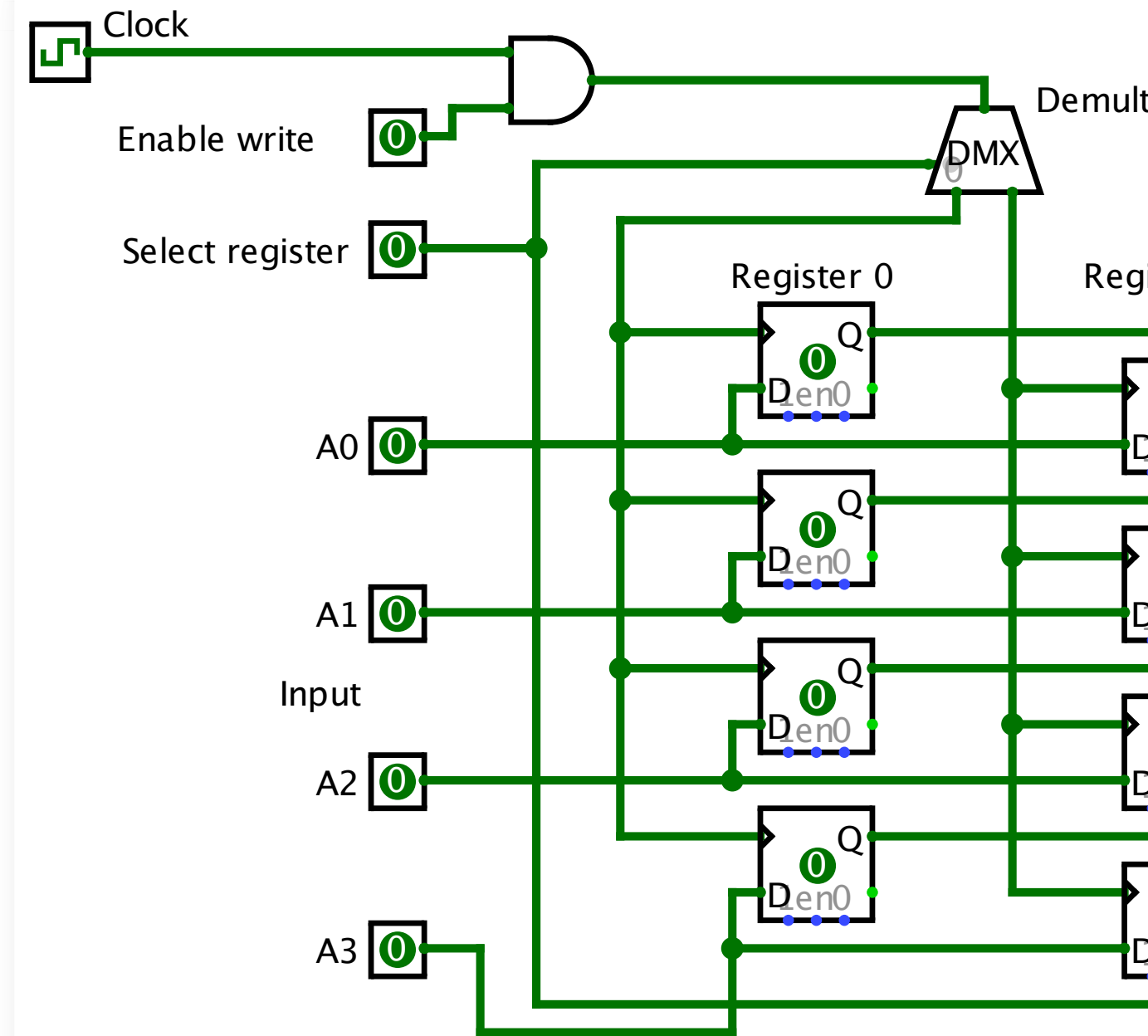

# Register file

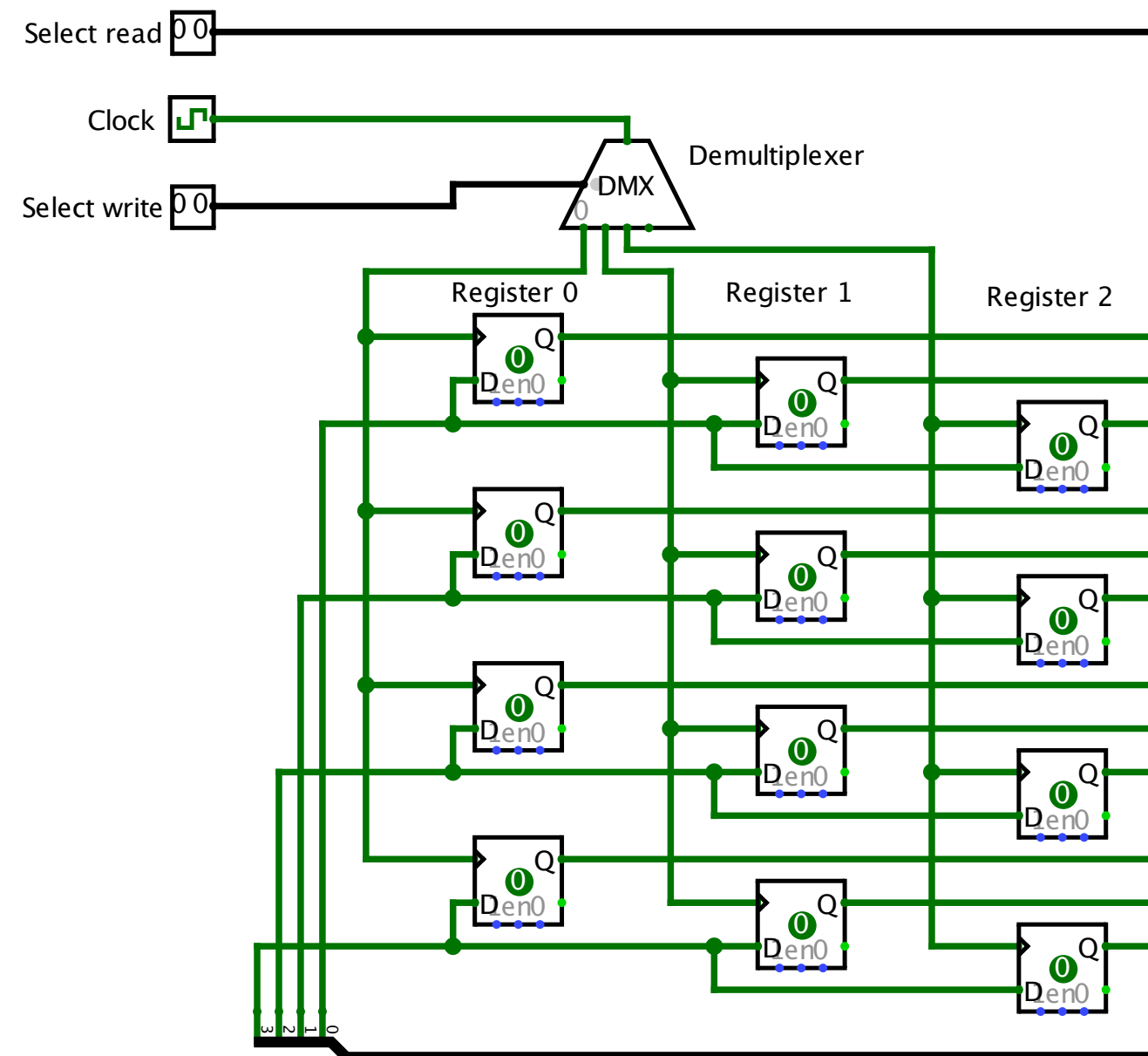

# Control

# Control

## (the machine)

# Control what?



# Control what?

- Fetch - decode - execute cycle

# Control what?

- Fetch - decode - execute cycle
- Implement the RTL code for each instruction
  - RTL = Register transfer language

# Control what?

- Fetch - decode - execute cycle
- Implement the RTL code for each instruction
  - RTL = Register transfer language
- Generate control signals for individual circuits
  - opcode for the ALU
  - read/write register number for the register file
  - memory read/write

# Timing

Let's take a look at the Add X instruction.

# Timing

Let's take a look at the Add X instruction.

- MAR X
  - register read control: IR (X is in IR)
  - register write control: MAR

# Timing

Let's take a look at the Add X instruction.

- MAR ← X
  - register read control: IR (X is in IR)
  - register write control: MAR
- MBR ← M[MAR]
  - memory: read (always reads at address MAR)
  - register write control: MBR

# Timing

Let's take a look at the Add X instruction.

- MAR ← X
  - register read control: IR (X is in IR)
  - register write control: MAR
- MBR ← M[MAR]
  - memory: read (always reads at address MAR)
  - register write control: MBR
- AC ← AC + MBR
  - ALU opcode: addition (always reads AC and MBR)
  - register write control: AC

# Timing

How do we generate that sequence of signals?

Add a cycle counter!

- $n$  outputs  $T_0$  to  $T_n$
- Cycle through these outputs at each clock cycle.
- Has an input  $C_n$  to reset to  $T_0$ .
- Now we can write RTL using Boolean statements!



# Cycle counter

# Cycle counter

# Control signals

- Register read:  $P_2$   $P_1$   $P_0$ 
  - Memory=0, MAR=1, PC=2, MBR=3, AC=4, IR=7
- Register write:  $P_5$   $P_4$   $P_3$
- ALU:  $A_1$   $A_0$ 
  - Add=1, Subt=2, Clear=3

# Add X with signals

MAR X

T<sub>3</sub> P<sub>3</sub> P<sub>2</sub> P<sub>1</sub> P<sub>0</sub>

# Add X with signals

MAR X

$T_3 \ P_3 \ P_2 \ P_1 \ P_0$

- read IR ( $P_2 = 1, P_1 = 1, P_0 = 1$ )

# Add X with signals

MAR X

$T_3 \ P_3 \ P_2 \ P_1 \ P_0$

- read IR ( $P_2 = 1, P_1 = 1, P_0 = 1$ )
- write MAR ( $P_5 = 0, P_4 = 0, P_3 = 1$ )

# Add X with signals

MAR X

$T_3$   $P_3$   $P_2$   $P_1$   $P_0$

- read IR ( $P_2 = 1, P_1 = 1, P_0 = 1$ )
- write MAR ( $P_5 = 0, P_4 = 0, P_3 = 1$ )

Note:  $T_0, T_1, T_2$  are used for the fetch cycle.

# Add X with signals

MBR   M[MAR]

$T_4$   $P_4$   $P_3$   $M_R$



# Add X with signals

MBR    $M[MAR]$

$T_4$   $P_4$   $P_3$   $M_R$

- Read memory (always reads at address MAR)

# Add X with signals

MBR    M[MAR]

$T_4$   $P_4$   $P_3$   $M_R$

- Read memory (always reads at address MAR)
- write MBR ( $P_5 = 0$ ,  $P_4 = 1$ ,  $P_3 = 1$ )

# Add X with signals

$AC \quad AC + MBR$

$T_5 \quad A_0 \quad P_5 \quad P_1 \quad P_0$

# Add X with signals

$AC \leftarrow AC + MBR$

$T_5 \quad A_0 \quad P_5 \quad P_1 \quad P_0$

- ALU: addition ( $A_1 = 0, A_0 = 1$ )

# Add X with signals

AC     $AC + MBR$

$T_5$   $A_0$   $P_5$   $P_1$   $P_0$

- ALU: addition ( $A_1 = 0, A_0 = 1$ )
- read MBR ( $P_2 = 0, P_1 = 1, P_0 = 1$ )

# Add X with signals

AC     $AC + MBR$

$T_5$   $A_0$   $P_5$   $P_1$   $P_0$

- ALU: addition ( $A_1 = 0, A_0 = 1$ )
- read MBR ( $P_2 = 0, P_1 = 1, P_0 = 1$ )
- write AC ( $P_5 = 1, P_4 = 0, P_3 = 0$ )

# Add X with signals

AC AC + MBR

$T_6$   $C_r$

# Add X with signals

$AC \leftarrow AC + MBR$


$T_6 \leftarrow C_r$

- reset cycle counter




# Control circuit (Add X)


# Control circuit (Add X)

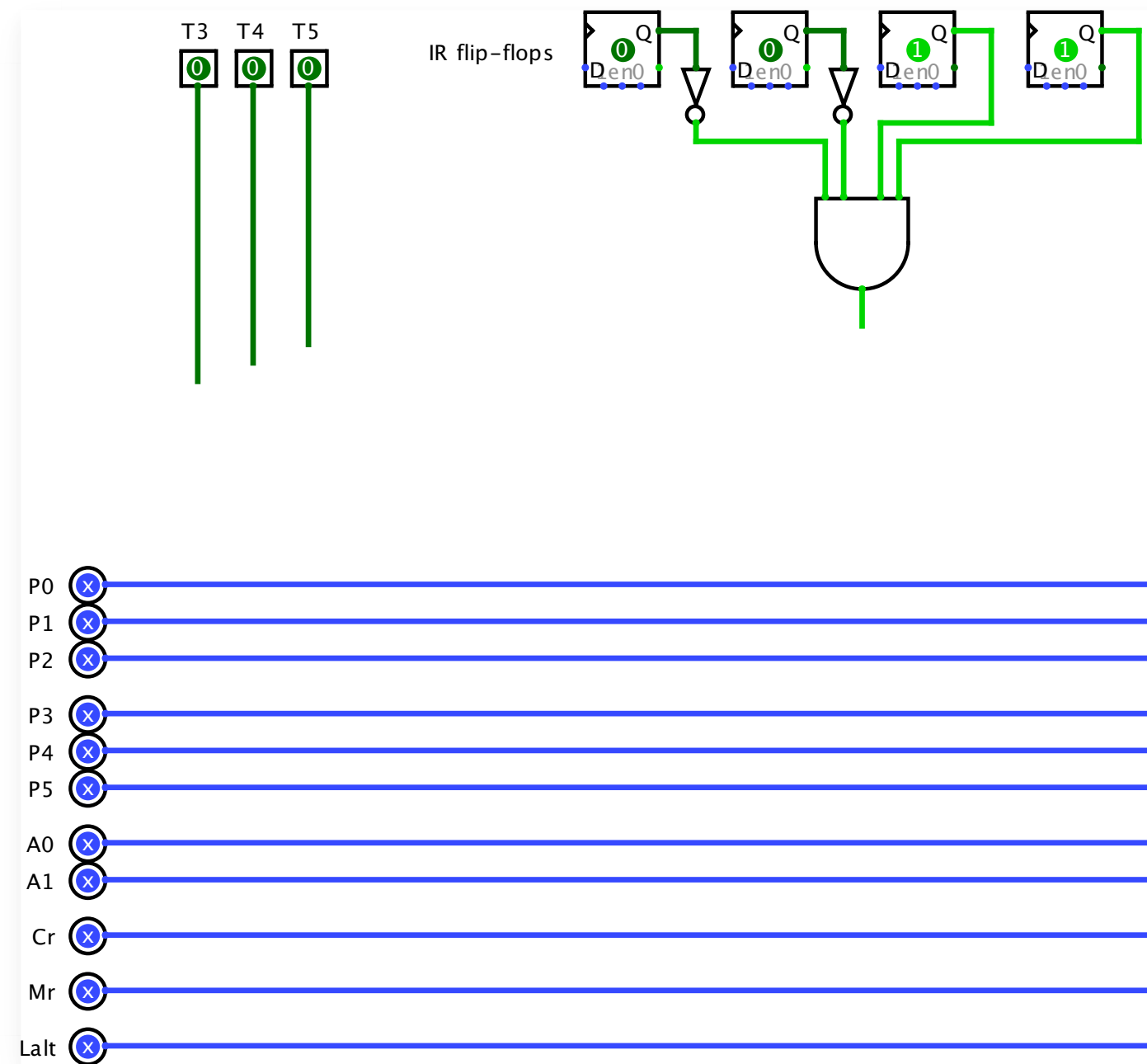


# Control circuit (Add X)

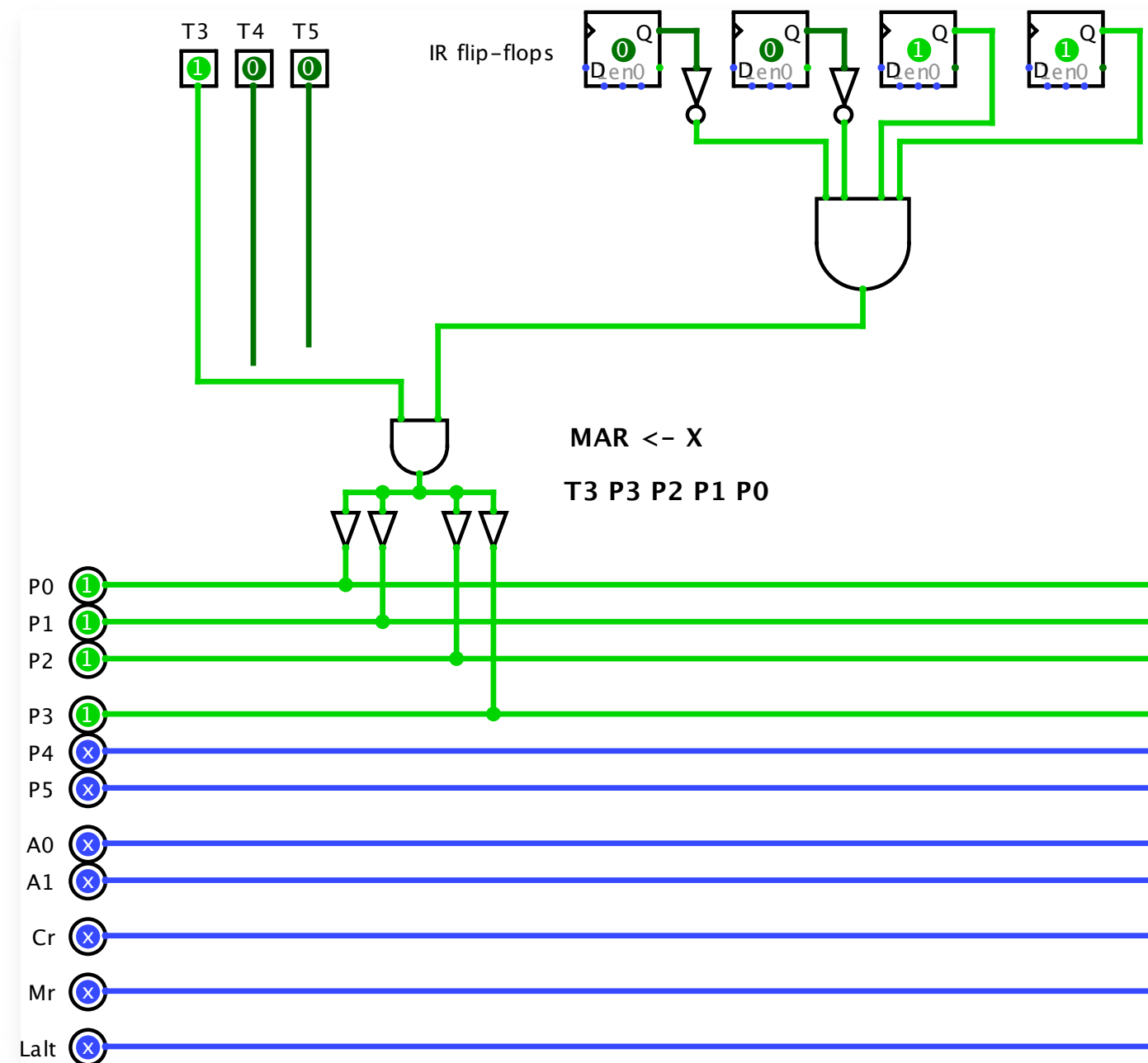


# Control circuit (Add X)

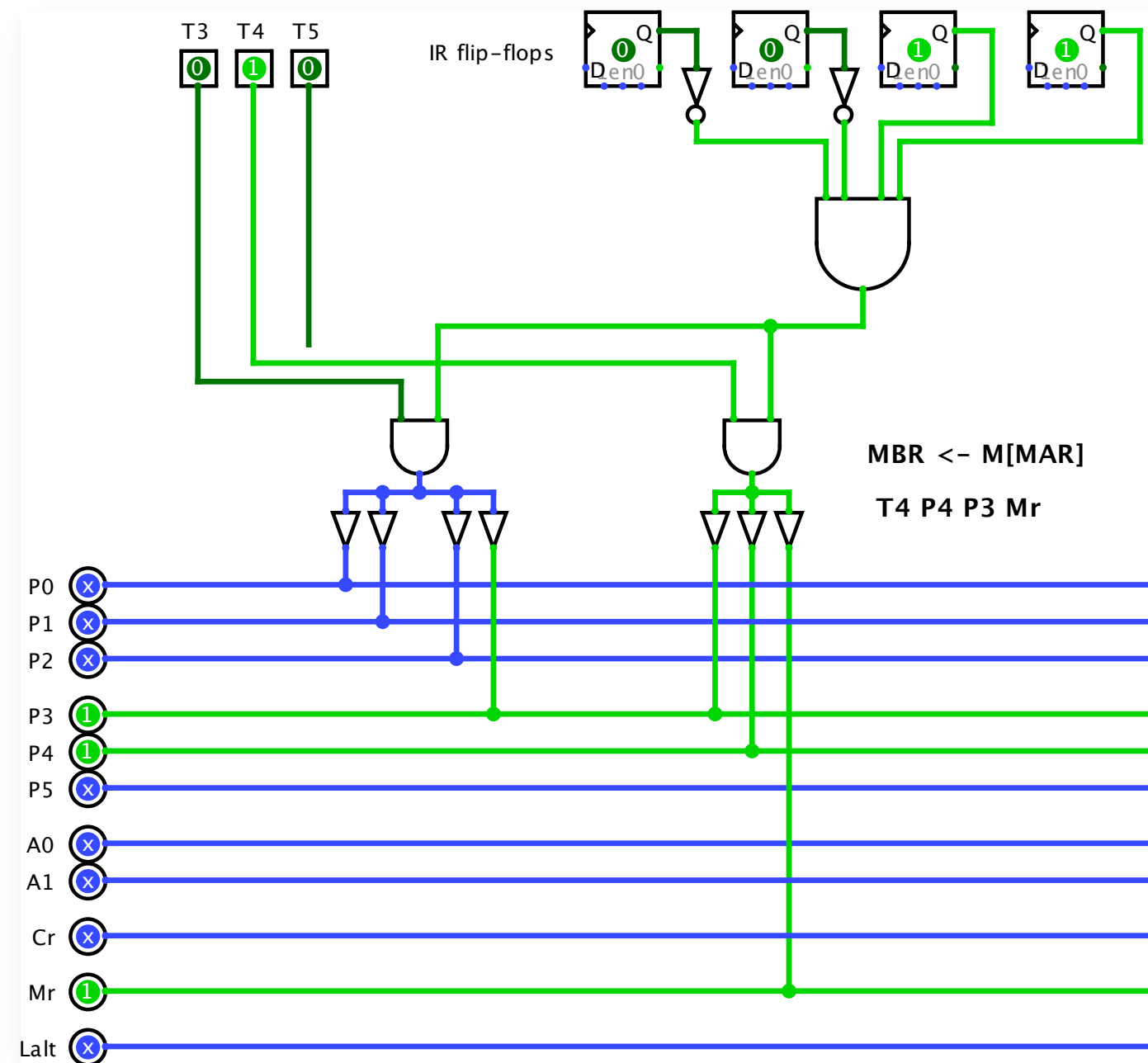

# Control circuit (Add X)

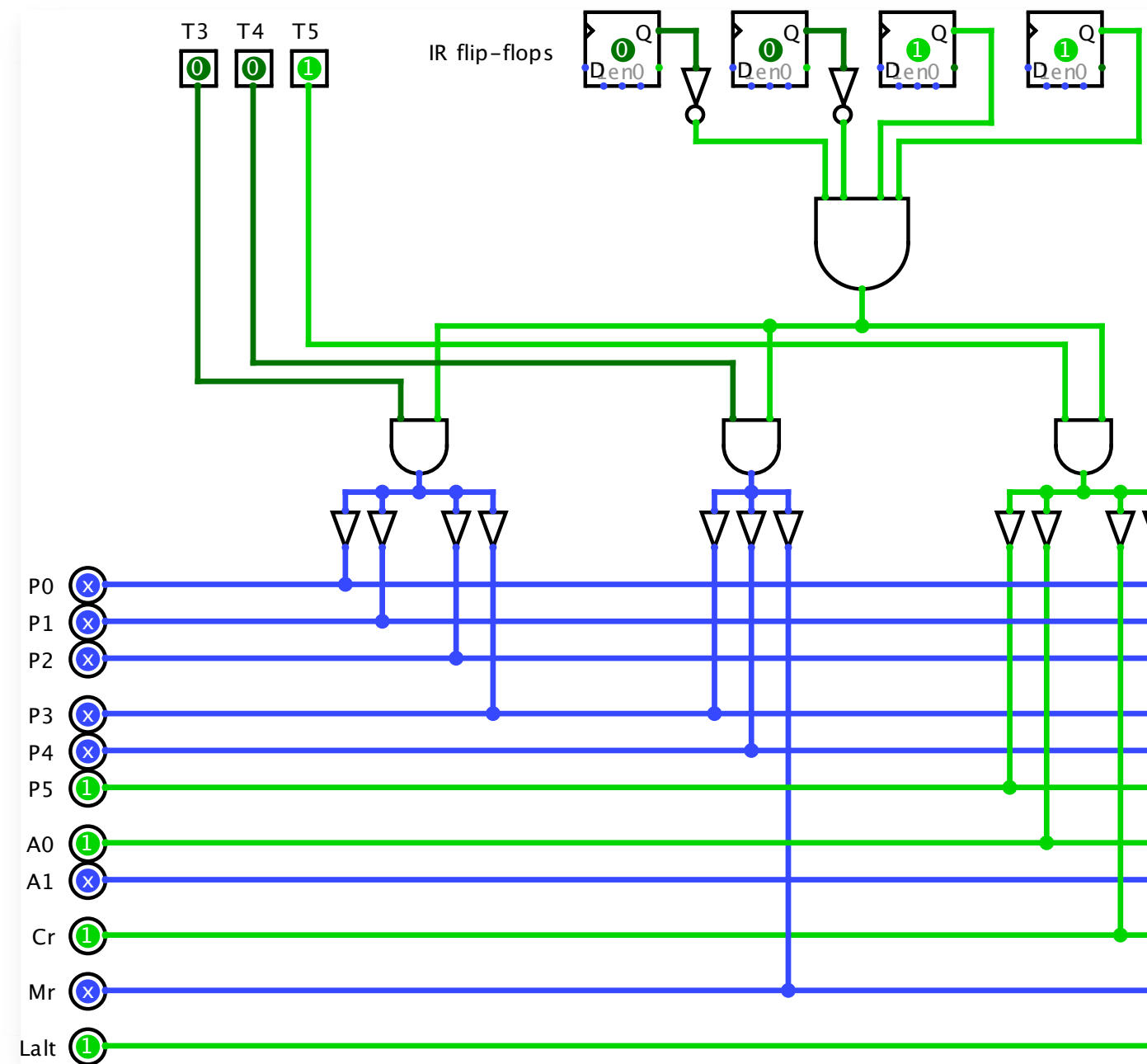

# Control circuit (Add X)

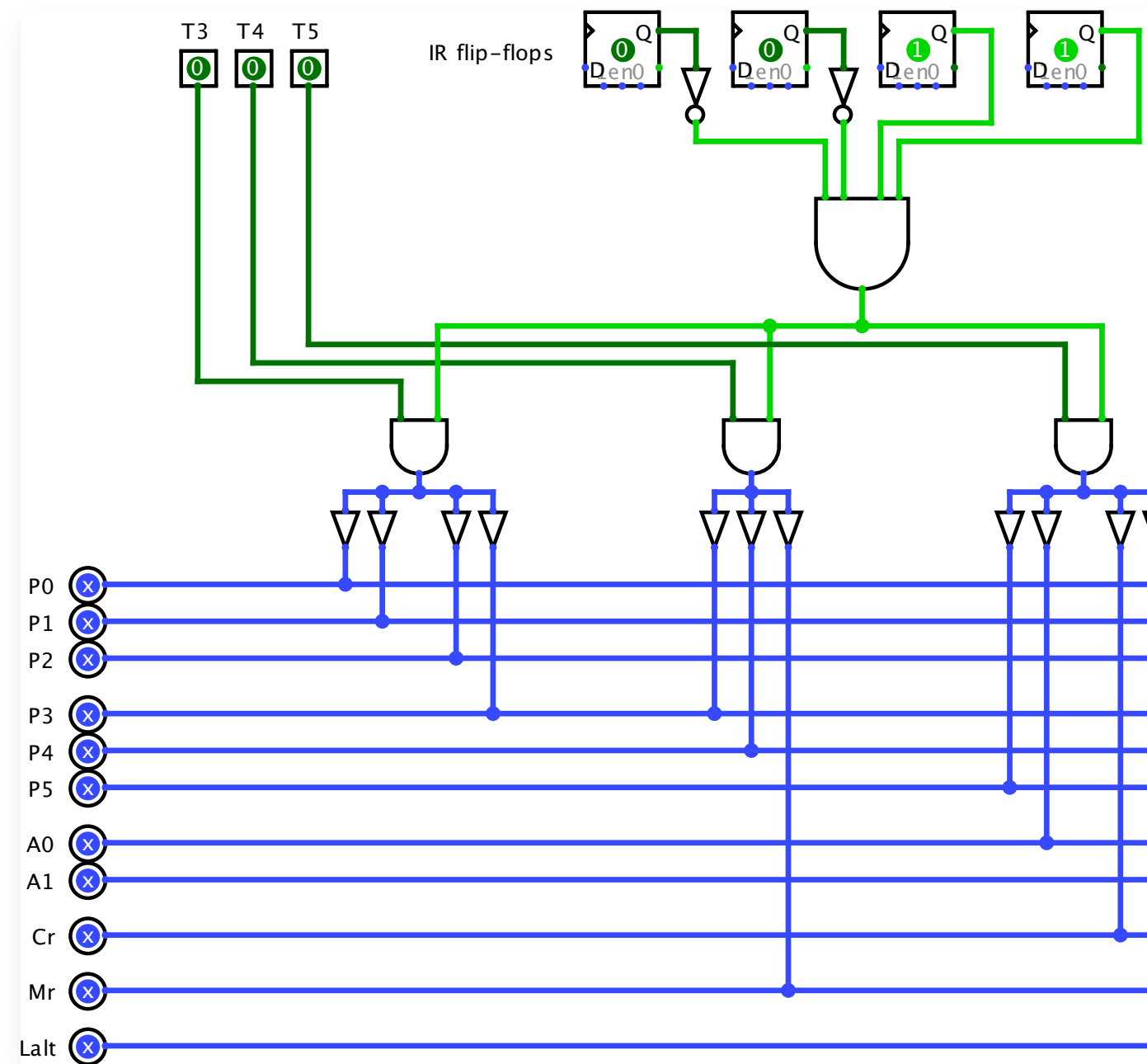

# Hardwired Control

RTL for each instruction is implemented using gates.

# Hardwired Control

RTL for each instruction is implemented using gates.

- Very fast!



# Hardwired Control

RTL for each instruction is implemented using gates.

- Very fast!
- But really complicated to design.

# Hardwired Control

RTL for each instruction is implemented using gates.

- Very fast!
- But really complicated to design.
- What if we want to add instructions?

# Hardwired Control

RTL for each instruction is implemented using gates.

- Very fast!
- But really complicated to design.
- What if we want to add instructions?
- What if we made a mistake?

# Microprogrammed Control

Break up instructions into microoperations.

# Microprogrammed Control

Break up instructions into microoperations.

- One microop per possible RTL instruction
  - Far fewer than instructions!

# Microprogrammed Control

Break up instructions into microoperations.

- One microop per possible RTL instruction
  - Far fewer than instructions!
- Microops for each instruction stored in memory in the processor

# Microprogrammed Control

Break up instructions into microoperations.

- One microop per possible RTL instruction
  - Far fewer than instructions!
- Microops for each instruction stored in memory in the processor
- Execution slightly slower, but
  - Circuits for microops much simpler
  - Microcode can be updated

# Putting it all together




# MARIE Data Paths

# MARIE Data Paths



**M**  
000  
001  
002  
003  
004  
005  
006

# MARIE Data Paths


 


M
000
001
002
003
004
005
006

# MARIE Data Paths

  


# MARIE Data Paths

  


Control


# MARIE Data Paths

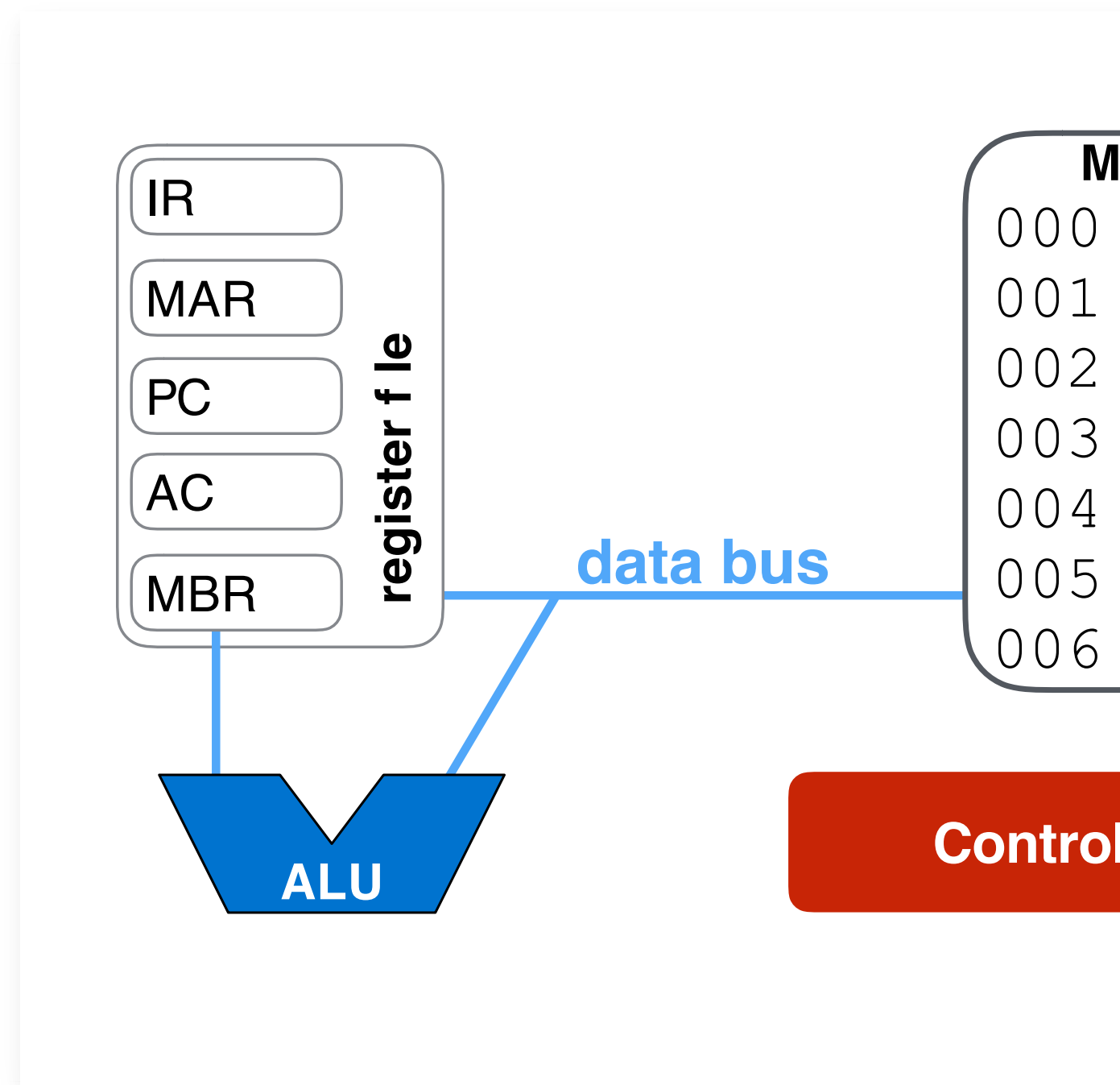

# MARIE Data Paths

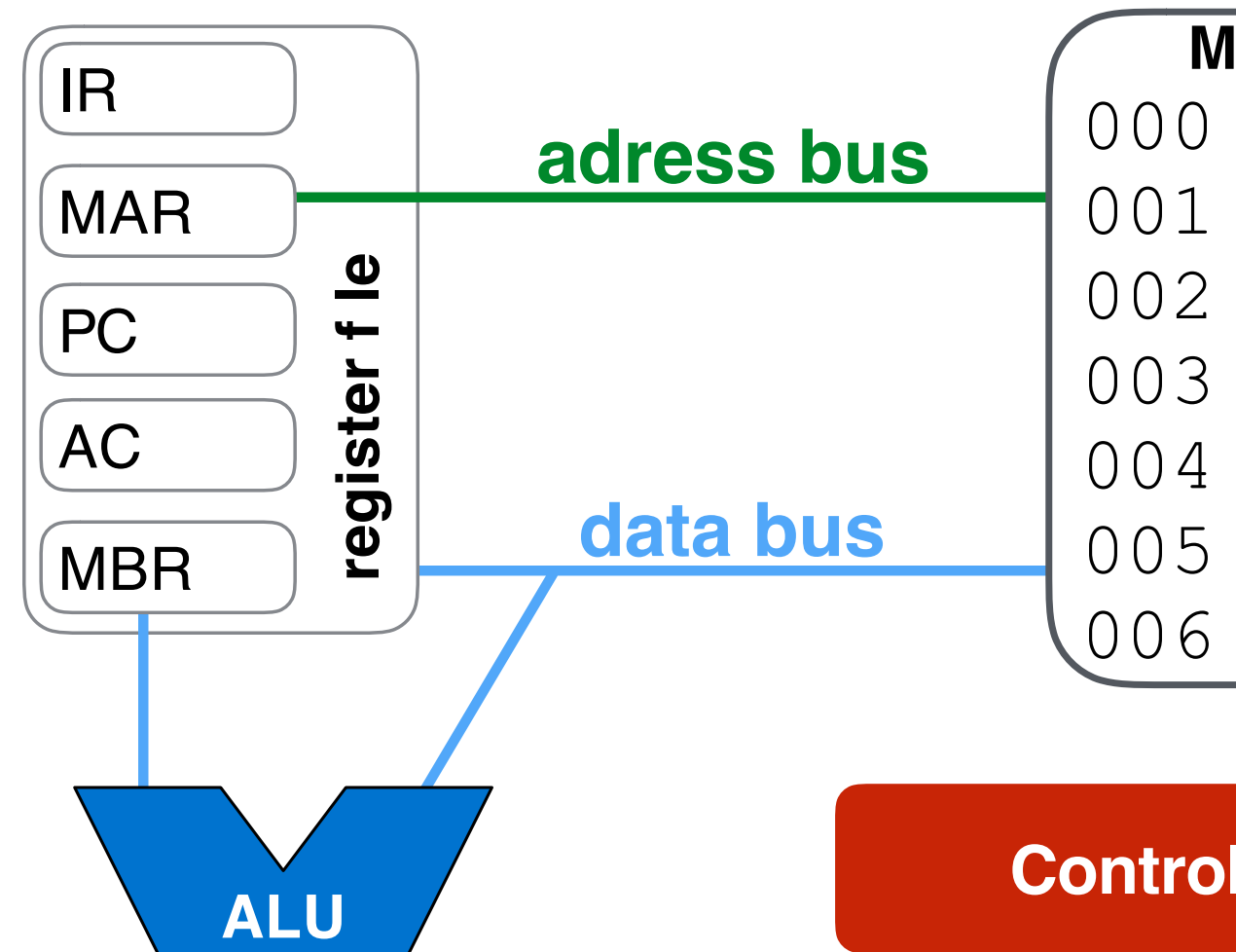

# MARIE Data Paths

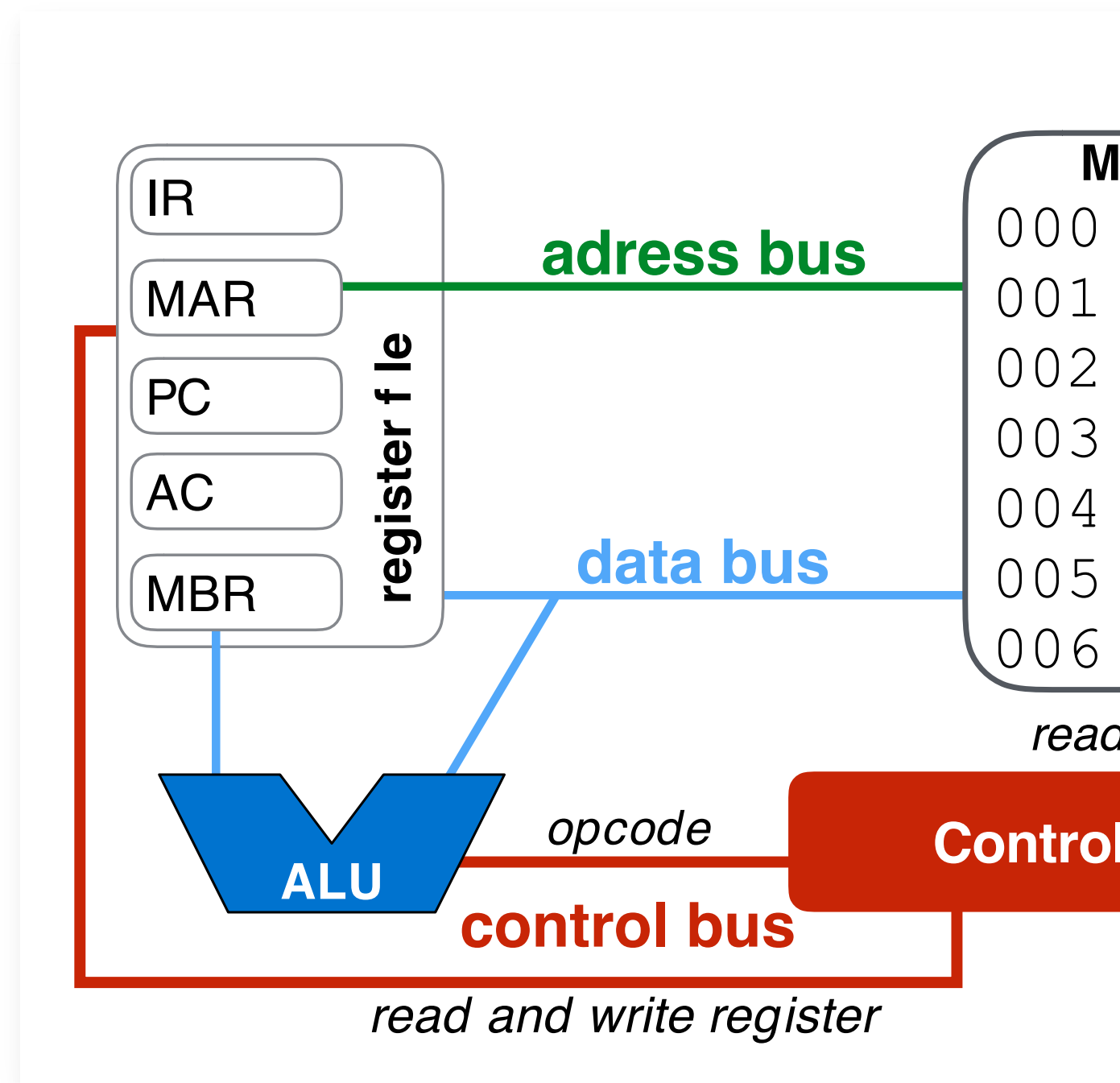



# Next lectures